

Figure 8.3: Virtual Lab connections of 4:1 Multiplexer

 


Figure 7.1: Seven segment display

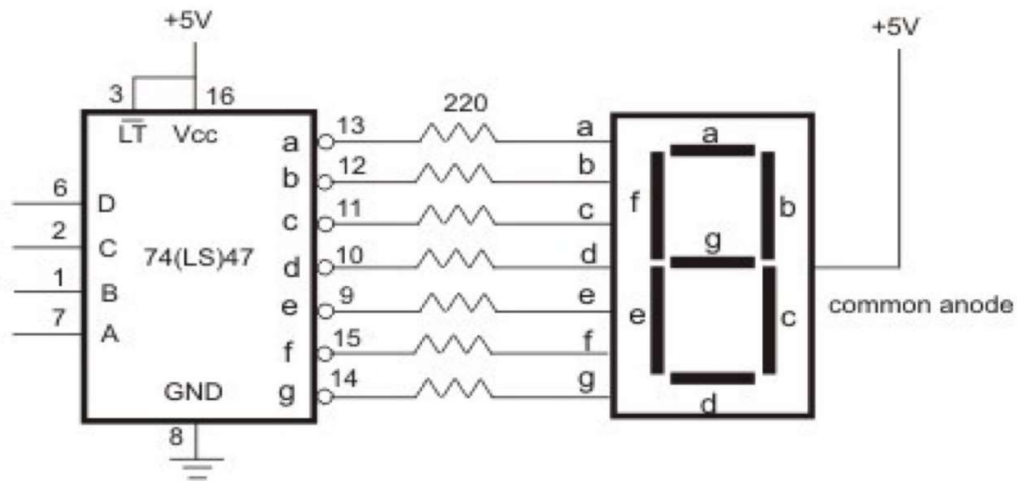


Figure 7.2: BCD to 7-segment display

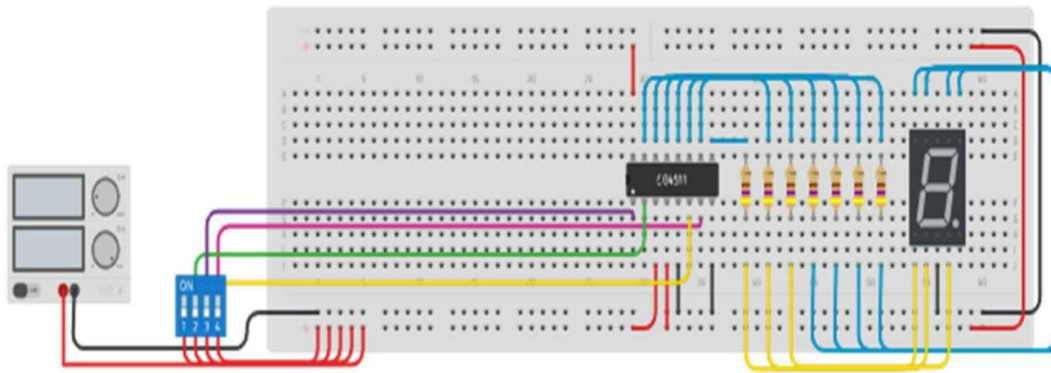


Figure 7.3: Breadboard connections

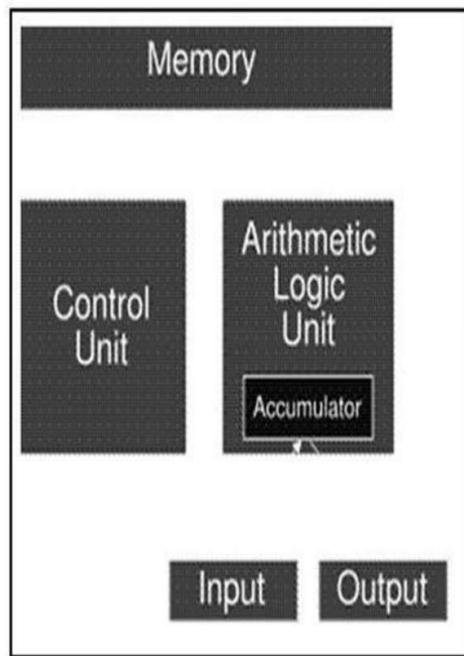


Figure 10.1: Central Processing Unit

 


Figure 10.2: Functional representation of ALU

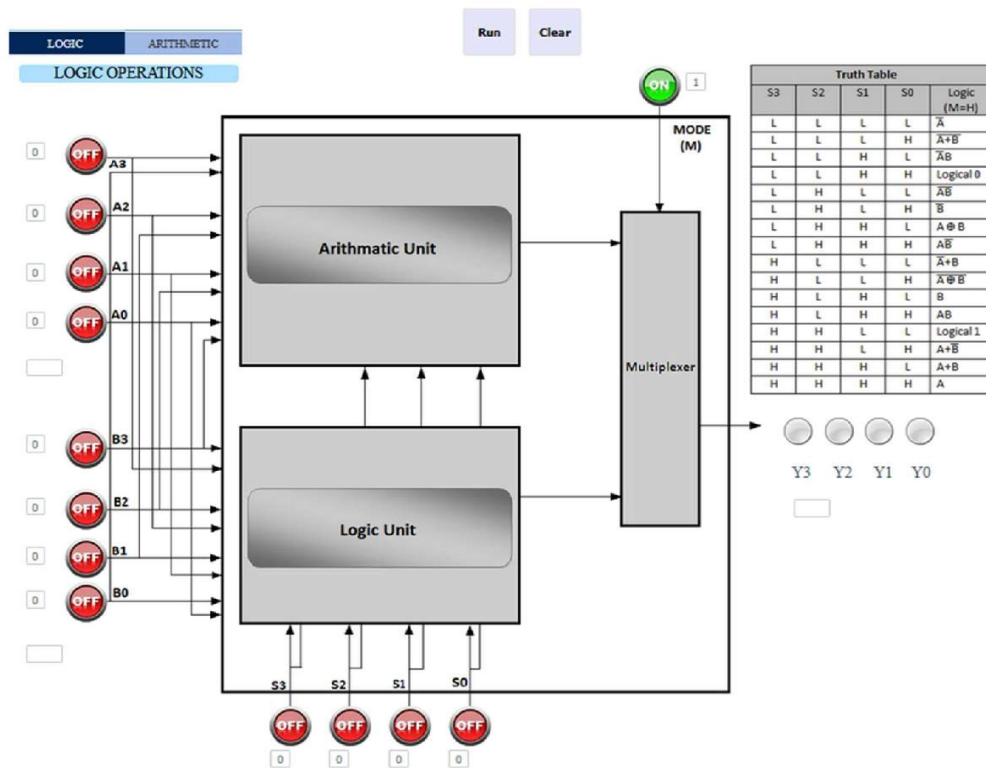


Figure 10.3: Simulation model for Logic Operations

 


Figure 10.4: Ex-OR Logic

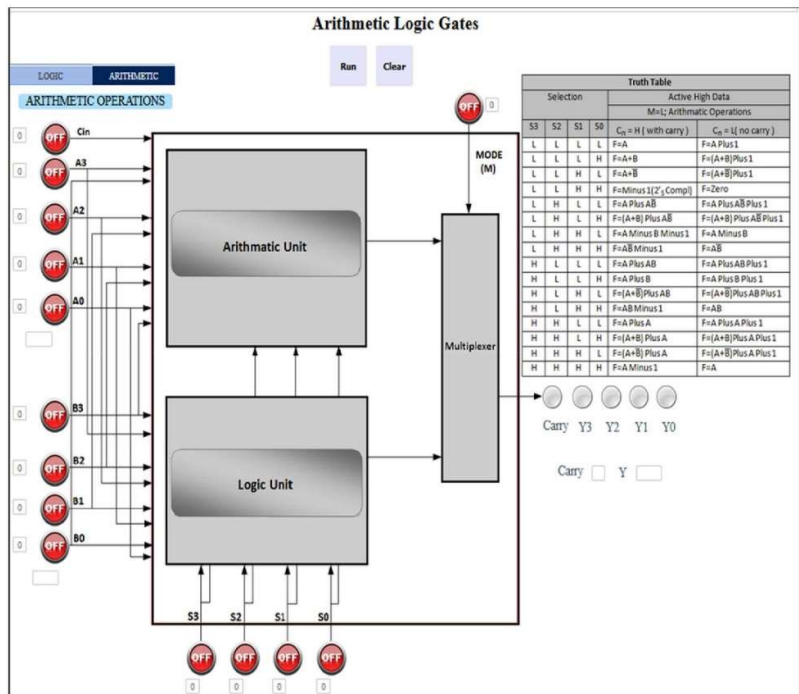


Figure 10.5: Simulation model for Arithmetic and Logic Operations

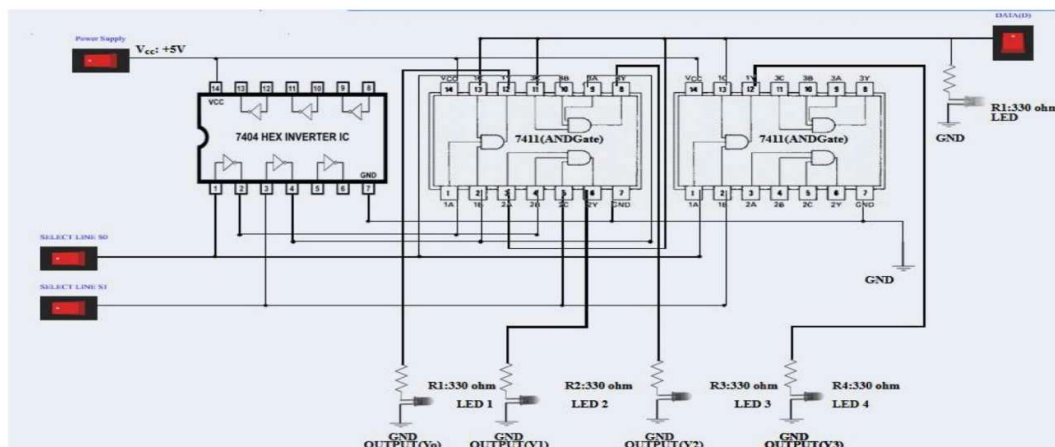


Figure. 8.4: Virtual Lab connections of 1:4 Demultiplexer

 


Figure. 8.5 Pin diagrams of IC 7411(3 input AND gate)

 


Figure. 8.6 Pin diagrams of IC 7432 (3 input OR gate)



The diagram shows a 4-bit parallel adder block, represented by a pink trapezoid. It has four data inputs on the left labeled D0, D1, D2, and D3. It has two select inputs at the bottom labeled S0 and S1. A single output line on the right is labeled "Output".

Figure 8.9: Breadboard connections of 1:4 Demultiplexer